

Introduction to VLSI Design Datapath

Tsung-Chu Huang
Electronics Eng., NCUE
2016/5/10

(I) Adders


- Single-bit Addition
- Carry-Ripple Adder
- Carry-Skip Adder
- Carry-Lookahead Adder
- Carry-Select Adder
- Carry-Increment Adder
- Tree Adder

2

Single-Bit Addition

Half Adder


$$S = A \oplus B$$
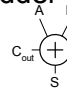
$$C_{out} = A \cdot B$$


A	B	C _{out}	S
0	0		
0	1		
1	0		
1	1		

Full Adder

$$S = A \oplus B \oplus C$$
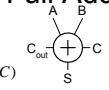
$$C_{out} = MAJ(A, B, C)$$


A	B	C	C _{out}	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

3

PGK

- For a full adder, define what happens to carries
 - (in terms of A and B)
 - Generate: $C_{out} = 1$ independent of C
 - ✓ $G = A \cdot B$
 - Propagate: $C_{out} = C$
 - ✓ $P = A \oplus B$
 - Kill: $C_{out} = 0$ independent of C
 - ✓ $K = \sim A \cdot \sim B$


4

Full Adder Design I

- Brute force implementation from eqns

$$S = A \oplus B \oplus C$$

$$C_{out} = MAJ(A, B, C)$$

 


5

Full Adder Design II

- Factor S in terms of C_{out}
 
$$S = ABC + (A + B + C)(\sim C_{out})$$
- Critical path is usually C to C_{out} in ripple adder



6

Layout


- Clever layout circumvents usual line of diffusion
- Use wide transistors on critical path
- Eliminate output inverters



7

Full Adder Design III

 
- Complementary Pass Transistor Logic (CPL)
- Slightly faster, but more area



8

Full Adder Design IV

 
- Dual-rail domino
- Very fast, but large and power hungry
- Used in very fast multipliers



9

Carry Propagate Adders

 - N-bit adder called CPA
 - Each sum bit depends on all previous carries
 - How do we compute all these carries quickly?




10

T.-C. HUANG, NCU

Carry-Ripple Adder

 - Simplest design: cascade full adders
 - Critical path goes from C_{in} to C_{out}
 - Design full adder to have fast carry delay




11

T.-C. HUANG, NCU

Inversions

 - Critical path passes through majority gate
 - Built from minority + inverter
 - Eliminate inverter and use inverting full adder



12

T.-C. HUANG, NCU

Generate / Propagate

- Equations often factored into G and P
- Generate and propagate for groups spanning i:j

$$G_{i:j} = G_{ik} + P_{ik} g G_{k-1:j}$$

$$P_{i:j} = P_{ik} g P_{k-1:j}$$

- Base case

$$G_{i:i} = G_i = A_i g B_i$$

$$G_{0:0} = G_0 = C_{in}$$

$$P_{i:i} = P_i = A_i \oplus B_i$$


$$P_{0:0} = P_0 = 0$$

- Sum: $S_i = P_i \oplus G_{i-1:0}$

13

T.-C. HUANG, NCU

PG Logic

 


14

T.-C. HUANG, NCU

Carry-Ripple Revisited

$$G_{i:0} = G_i + P_i g G_{i-1:0}$$

 


15

T.-C. HUANG, NCU

Carry-Ripple PG Diagram

 
$$t_{ripple} = t_{pg} + (N-1)t_{AO} + t_{xor}$$



16

T.-C. HUANG, NCU

PG Diagram Notation

 


17

T.-C. HUANG, NCU

Carry-Skip Adder

 
- Carry-ripple is slow through all N stages
- Carry-skip allows carry to skip over groups of n bits
 - Decision based on n-bit propagate signal



18

T.-C. HUANG, NCU

Carry-Skip PG Diagram

 


$$t_{\text{skip}} = t_{pg} + [2(n-1) + (k-1)]t_{AO} + t_{xor}$$

For k n-bit groups (N = nk)

19

T.-C. HUANG, NCU

Variable Group Size

 


Delay grows as $O(\sqrt{\text{sgt}(N)})$

20

T.-C. HUANG, NCU

Carry-Lookahead Adder

 
- Carry-lookahead adder computes $G_{i:0}$ for many bits in parallel.
- Uses higher-valency cells with more than two inputs.



21

T.-C. HUANG, NCU


CLA PG Diagram

 

22

T.-C. HUANG, NCU

Higher-Valency Cells

 


23

T.-C. HUANG, NCU

Carry-Select Adder

 - Trick for critical paths dependent on late input X
 - Precompute two possible outputs for $X = 0, 1$
 - Select proper output when X arrives
- Carry-select adder precomputes n-bit sums
 - For both possible carries into n-bit group




24

T.-C. HUANG, NCU

Carry-Increment Adder

 - Factor initial PG and final XOR out of carry-select




$$t_{\text{increment}} = t_{pg} + [(n-1) + (k-1)]t_{AO} + t_{xor}$$

25

T.-C. HUANG, NCU

Variable Group Size

- Also buffer noncritical signals

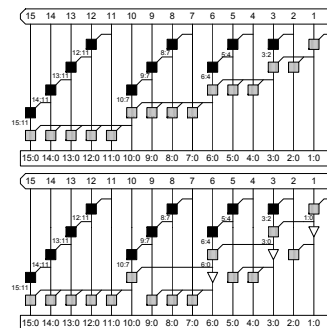

26

T.-C. HUANG, NCU


Tree Adder

- If lookahead is good, lookahead across lookahead!
 - Recursive lookahead gives $O(\log N)$ delay
- Many variations on tree adders

27

T.-C. HUANG, NCU


Brent-Kung

 

28

T.-C. HUANG, NCU


Sklansky

 

29

T.-C. HUANG, NCU

Kogge-Stone

 

30

T.-C. HUANG, NCU


Tree Adder Taxonomy

- Ideal N-bit tree adder would have
 - $L = \log N$ logic levels
 - Fanout never exceeding 2
 - No more than one wiring track between levels
- Describe adder with 3-D taxonomy (l, f, t)
 - Logic levels: $L + l$
 - Fanout: $2^l + 1$
 - Wiring tracks: 2^l
- Known tree adders sit on plane defined by $l + f + t = L - 1$

31

T.-C. HUANG, NCU


Tree Adder Taxonomy

 

32

T.-C. HUANG, NCU


Han-Carlson

 

33

T.-C. HUANG, NCU


Knowles [2, 1, 1, 1]

 

34

T.-C. HUANG, NCU


Ladner-Fischer

 

35

T.-C. HUANG, NCU

Taxonomy Revisited

 

36

T.-C. HUANG, NCU

Summary

Adder architectures offer area / power / delay tradeoffs.
Choose the best one for your application.

Architecture	Classification	Logic Levels	Max Fanout	Tracks	Cells
Carry-Ripple		N-1	1	1	N
Carry-Skip n=4		N/4 + 5	2	1	1.25N
Carry-Inc. n=4		N/4 + 2	4	1	2N
Brent-Kung	(L-1, 0, 0)	$2\log_2 N - 1$	2	1	2N
Skiansky	(0, L-1, 0)	$\log_2 N$	N/2 + 1	1	$0.5 N \log_2 N$
Kogge-Stone	(0, 0, L-1)	$\log_2 N$	2	N/2	$N \log_2 N$

37

T.-C. HUANG, NCUÉ

(II) Basic Functions of Datapath

- Comparators
- Shifters
- Multi-input Adders
- Multipliers

38

T.-C. HUANG, NCUÉ

Comparators


- 0's detector: $A = 00\dots000$
- 1's detector: $A = 11\dots111$
- Equality comparator: $A = B$
- Magnitude comparator: $A < B$

39

T.-C. HUANG, NCUÉ

1's & 0's Detectors

 - 1's detector: N-input AND gate
- 0's detector: NOTs + 1's detector (N-input NOR)




40

T.-C. HUANG, NCUÉ

Equality Comparator

 - Check if each bit is equal (XNOR, aka equality gate)
- 1's detect on bitwise equality




41

T.-C. HUANG, NCUÉ

Magnitude Comparator

 - Compute $B - A$ and look at sign
- $B - A = B + \sim A + 1$
- For unsigned numbers, carry out is sign bit



42

T.-C. HUANG, NCUÉ

Signed vs. Unsigned

- For signed numbers, comparison is harder
 - C: carry out
 - Z: zero (all bits of $B - A$ are 0)
 - N: negative (MSB of result)
 - V: overflow (inputs had different signs, output sign \neq B)
 - S: N xor V (sign of result)

Relation	Unsigned Comparison	Signed Comparison
$A = B$	Z	Z
$A \neq B$	\bar{Z}	\bar{Z}
$A < B$	$C + \bar{Z}$	$\bar{S} \cdot \bar{Z}$
$A > B$	C	S
$A \leq B$	\bar{C}	\bar{S}
$A \geq B$	$\bar{C} + Z$	$S + Z$

43

T.-C. HUANG, NCUÉ

Shifters


- Logical Shift:
 - Shifts number left or right and fills with 0's
 - ✓ 1011 LSR 1 = 0101 1011 LSL 1 = 0110
- Arithmetic Shift:
 - Shifts number left or right. Rt shift sign extends
 - ✓ 1011 ASR 1 1011 ASL 1
- Rotate:
 - Shifts number left or right and fills with lost bits
 - ✓ 1011 ROR 1 = 1101 1011 ROL 1 = 0111

44

T.-C. HUANG, NCUÉ

Funnel Shifter

 - A funnel shifter can do all six types of shifts
- Selects N-bit field Y from $2N-1$ -bit input
 - Shift by k bits ($0 \leq k < N$)
 - Logically involves N N:1 multiplexers



45

T.-C. HUANG, NCUÉ

Funnel Source Generator


Shift Type	$Z_{2N-2:N}$	Z_{N-1}	$Z_{N-2:0}$	Offset
Rotate Right	$A_{N-2:0}$	A_{N-1}	$A_{N-2:0}$	k
Logical Right	0	A_{N-1}	$A_{N-2:0}$	k
Arithmetic Right	sign	A_{N-1}	$A_{N-2:0}$	k
Rotate Left	$A_{N-1:1}$	A_0	$A_{N-1:1}$	\bar{k}
Logical/Arithmetic Left	$A_{N-1:1}$	A_0	0	\bar{k}

46

T.-C. HUANG, NCU

Array Funnel Shifter

 - N N-input multiplexers
- Use 1-of-N hot select signals for shift amount
- nMOS pass transistor design (V_t drops!)




47

T.-C. HUANG, NCU

Logarithmic Funnel Shifter

 - Log N stages of 2-input muxes
- No select decoding needed




48

T.-C. HUANG, NCU

32-bit Logarithmic Funnel

 - Wider multiplexers reduce delay and power
- Operands > 32 bits introduce datapath irregularity



49

T.-C. HUANG, NCU


Barrel Shifter

- Barrel shifters perform right rotations using wrap-around wires.
- Left rotations are right rotations by $N - k = k + 1$ bits.
- Shifts are rotations with the end bits masked off.

50

T.-C. HUANG, NCU

Logarithmic Barrel Shifter

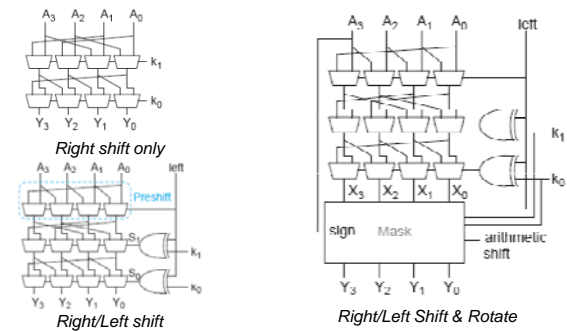


51

T.-C. HUANG, NCU

32-bit Logarithmic Barrel

 - Datapath never wider than 32 bits
- First stage preshifts by 1 to handle left shifts




52

T.-C. HUANG, NCU

Multi-input Adders

 - Suppose we want to add k N-bit words
- Ex: $0001 + 0111 + 1101 + 0010 = 10111$
- Straightforward solution: k-1 N-input CPAs
- Large and slow




53

T.-C. HUANG, NCU

Carry Save Addition

 - A full adder sums 3 inputs and produces 2 outputs
- Carry output has twice *weight* of sum output
- N full adders in parallel are called *carry save adder*
- Produce N sums and N carry outs




54

T.-C. HUANG, NCU

CSA Application

 - Use k-2 stages of CSAs
 - Keep result in carry-save redundant form
- Final CPA computes actual result



55

T.-C. HUANG, NCU

Multiplication

- Example:

$$\begin{array}{r}
 1100 : 12_{10} \\
 0101 : 5_{10} \\
 \hline
 1100 \\
 0000 \\
 1100 \\
 0000 \\
 \hline
 00111100 : 60_{10}
 \end{array}$$

multiplicand
 multiplier
 partial products
 product

- M x N-bit multiplication
 - Produce N M-bit partial products
 - Sum these to produce M+N-bit product


56

T.-C. HUANG, NCU

General Form

- Multiplicand: $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$
- Multiplier: $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$
 
$$\text{Product } P = \left(\sum_{j=0}^{M-1} y_j 2^j \right) \left(\sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$




57

T.-C. HUANG, NCU

Dot Diagram


- Each dot represents a bit

 

58

T.-C. HUANG, NCU

Array Multiplier

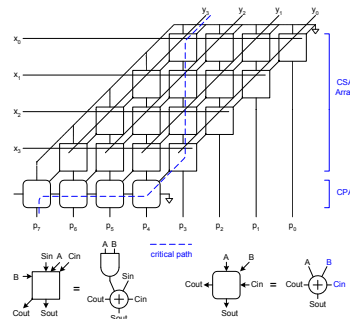


59

T.-C. HUANG, NCU

Rectangular Array

 - Squash array to fit rectangular floorplan



60

T.-C. HUANG, NCU

Fewer Partial Products

- Array multiplier requires N partial products
- If we looked at groups of r bits, we could form N/r partial products.
 - Faster and smaller?
 - Called radix-2^r encoding
- Ex: r = 2: look at pairs of bits
 - Form partial products of 0, Y, 2Y, 3Y
 - First three are easy, but 3Y requires adder

61

T.-C. HUANG, NCU

Booth Encoding

- Instead of 3Y, try -Y, then increment next partial product to add 4Y
- Similarly, for 2Y, try -2Y + 4Y in next partial product


Inputs			Partial Product	Booth Selects		
x_{2i+1}	x_{2i}	x_{2i-1}	PP_i	SINGLE _i	DOUBLE _i	NEG _i
0	0	0	0	0	0	0
0	0	1	Y	1	0	0
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

62

T.-C. HUANG, NCU

Booth Hardware

 - Booth encoder generates control lines for each PP
 - Booth selectors choose PP bits



63

T.-C. HUANG, NCU

An 8-bit Booth Multiplier in Verilog

```

module multiplier(prod, busy, mc, mp, clk, start);
output [15:0] prod; output busy;
input [7:0] mc, mp; input clk, start;
reg [7:0] A, Q, M; reg Q_1;
reg [3:0] count;
wire [7:0] sum, difference;
always @(posedge clk)
begin
if (start) begin A <= 8'b0;
M <= mc;
Q <= mp;
Q_1 <= 1'b0;
count <= 4'b0;
end else begin
case ({Q[0], Q_1})
2'b01 : {A, Q, Q_1} <= {sum[7], sum, Q};
2'b10 : {A, Q, Q_1} <= {difference[7],
difference, Q};
default : {A, Q, Q_1} <= {A[7], A, Q};
endcase
endcase
count <= count + 1'b1;
end
end
alu adder (sum, A, M, 1'b0);
alu subtractor (difference, A, ~M, 1'b1);
assign prod = {A, Q};
assign busy = (count < 8);
endmodule


```

64

T.-C. HUANG, NCU

Sign Extension

 - Partial products can be negative
 - Require sign extension, which is cumbersome
 - High fanout on most significant bit




65

T.-C. HUANG, NCU

Simplified Sign Ext.

 - Sign bits are either all 0's or all 1's
 - Note that all 0's is all 1's + 1 in proper column
 - Use this to reduce loading on MSB




66

T.-C. HUANG, NCU

Even Simpler Sign Ext.

 - No need to add all the 1's in hardware
 - Precompute the answer!



67

T.-C. HUANG, NCU

Advanced Multiplication

- Signed vs. unsigned inputs
- Higher radix Booth encoding
- Array vs. tree CSA networks

68

T.-C. HUANG, NCU


(III) Advanced Datapaths

- Division (y/x): shift + Add/Sub
- Reciprocal ($1/x$): Newton's Method
- Multiplier: Shifter + Parallel Adder
- Square-Root (\sqrt{x}): Babylonian Method
- $\cos(x)$, $\sin(x)$: CORDIC Algorithm
- $\exp(x)$, $\log(x)$: CORDIC Algorithm

69

T.-C. HUANG, NCU

Time-Space Complexity

 

70

T.-C. HUANG, NCU

General Coordinate Rotation Digital Computation

- Vector function $f(x) = f(x - x_i) \cdot g(x_i)$
- $g(x_i) = d_{i0}2^0 + d_{i1}2^1 + d_{i2}2^2 + \dots + d_{im_i}2^{m_i}$
- The fewer items the finer!
 - Basic CORDIC fine vector: $\begin{pmatrix} 1 & -2^{m_i} \\ 2^{m_i} & 1 \end{pmatrix}$
 - Fine numbers for exp, log: $2^0 + 2^{m_i}$
- One end is precise.
- Convergence
- Convergence rate is efficient.
 - dichotomy

71

T.-C. HUANG, NCU

CORDIC-Able Functions

- All standard, inverse, hyperbolic trigonometric functions
- All linear combinations of trigonometric functions are potential "cordicible"

72

T.-C. HUANG, NCU

Algorithm → C Code → Verilog Code

```
#define K 0x26DD3B6A
#define half_pi 0x6487ED51
int Tab[] = {0x3243F6A8, 0x1DAC6705, 0x0FADBAFC, 0x07F56EA6,
0x03FEAB76, 0x01FFD55B,
0x00FFFAAA, 0x007FFF55, 0x003FFFEA, 0x001FFFFD, 0x000FFFFF,
0x0007FFFF, 0x0003FFFF,
0x0001FFFF, 0x0000FFFF, 0x00007FFF, 0x00003FFF, 0x00001FFF,
0x00000FFF, 0x000007FF,
0x000003FF, 0x000001FF, 0x000000FF, 0x0000007F, 0x0000003F,
0x0000001F, 0x0000000F,
0x00000008, 0x00000004, 0x00000002, 0x00000001, 0x00000000, };

void cordic(int theta, int *s, int *c, int n)
{
    int k, d, tx, ty, tz;
    int x=K,y=0,z=theta;
    for (k=0; k<n; ++k)
    {
        d = z>>31;
        tx = x - (((y>>k) ^ d) - d);
        ty = y + (((x>>k) ^ d) - d);
        tz = z - ((Tab[k] ^ d) - d);
        x = tx; y = ty; z = tz;
    }
    *c = x; *s = y;
}
```

73

T.-C. HUANG, NCUÉ

Algorithm → C Code → Verilog Code

```
module CORDIC32(Clk, Rst, theta, sin, cos);
input Clk, Rst;
input [31:0] theta; // angle in fixed-point <2.30>
output [31:0] sin, cos; // sine and cosine in <2.30>

reg [31:0] sin, cos, phi, A;
reg [5:0] k;
wire [31:0] sin2k, cos2k, delta_sin, delta_cos, delta_A;
assign sin2k = sin[31] ? ~((-sin)>>k) : sin >> k;
assign cos2k = cos[31] ? ~((-cos)>>k) : cos >> k;
assign delta_sin = phi[31] ? (~sin2k + 1) : sin2k;
assign delta_cos = phi[31] ? (~cos2k + 1) : cos2k;
assign delta_A = phi[31] ? (~A + 1) : A;

always@(posedge Clk)
if(Rst)
begin
    phi <= theta;
    sin <= 32'h00000000;
    cos <= 32'h26DD3B6A;
    k <= 0;
end
else
if(!k[5])
begin
    cos <= cos - delta_sin;
    sin <= sin + delta_cos;
    phi <= phi - delta_A;
    k <= k + 1;
end
end
begin
end
```

74

T.-C. HUANG, NCUÉ

Algorithm → C Code → Verilog Code


```
always@(*)
case(k[4:0])
0: A = 32'h3243F6A8;
1: A = 32'h1DAC6705;
2: A = 32'h0FADBAFC;
3: A = 32'h07F56EA6;
4: A = 32'h03FEAB76;
5: A = 32'h01FFD55B;
6: A = 32'h00FFFAAA;
7: A = 32'h007FFF55;
8: A = 32'h003FFFEA;
9: A = 32'h001FFFFD;
10: A = 32'h000FFFFF;
11: A = 32'h0007FFFF;
12: A = 32'h0003FFFF;
13: A = 32'h0001FFFF;
14: A = 32'h0000FFFF;
15: A = 32'h00007FFF;
16: A = 32'h00003FFF;
17: A = 32'h00001FFF;
18: A = 32'h00000FFF;
19: A = 32'h000007FF;
20: A = 32'h000003FF;
21: A = 32'h000001FF;
22: A = 32'h000000FF;
23: A = 32'h0000007F;
24: A = 32'h0000003F;
25: A = 32'h0000001F;
26: A = 32'h0000000F;
27: A = 32'h00000008;
28: A = 32'h00000004;
29: A = 32'h00000002;
30: A = 32'h00000001;
31: A = 32'h00000000;
endcase
endmodule
```

75

T.-C. HUANG, NCUÉ

Fast Fourier Transform (FFT)

Decimation in Frequency (DIF)

 


76

T.-C. HUANG, NCUÉ

Fast Fourier Transform (FFT)


Decimation in Time (DIT)

 

77

T.-C. HUANG, NCUÉ

Infinite-Impulse-Response (IIR) Filter

 

78

T.-C. HUANG, NCUÉ