

VLSI Design

Tsung-Chu Huang

Department of Electronic Engineering
National Changhua University of Education
Email: tch@cc.ncue.edu.tw

2016/05/10

Sequential Circuits


A. Asynchronous

1. Extremely large set! Even synchronous circuits are usually considered as asynchronous circuits in general sense.
2. For some applications, the delay of signals can be looked as a small D-FF and they are usually designed according to Huffman model.
3. Some specials: self-time logics, hand-shaking, bi-directional, etc.

B. Synchronous

1. **Single Clock**
 1. Single Phase
 - 1C1P DFF Array-based Finite State Machine
 - The rest can be transferred to the DFF-based
 - Most popular and easy to design
 2. Complemented Phase, Double-edge-triggered, Double-data-rate
 3. Multiple phase (exclusive pulses)
2. **Multiple Clocks**
 1. Clock domain interfacing, complicated!

Implementations of 1C1PD-FSM

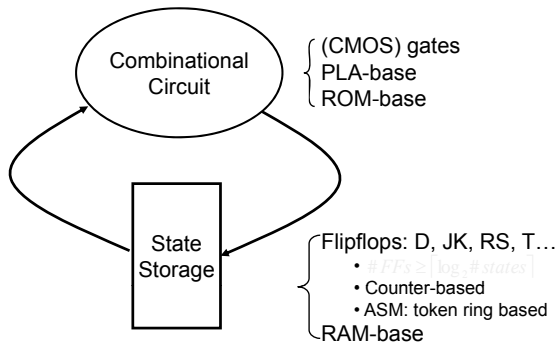

Example: Flipflops

➤ Positive-Edge Triggered D-Flipflop:

```
module DFF(Clk, D, Q);
  input Clk, D;
  output Q;
  reg Q;
  always@(posedge Clk)
    Q=D;
endmodule
```

➤ Resettable DFF: (Asynchronous)

```
module DFF(Rst, Clk, D, Q);
  input Rst, Clk, D;
  output Q;
  reg Q;
  always@(posedge Clk or posedge Rst)
    if (Rst) Q=1'b0;
    else Q=D;
endmodule
```

➤ Resettable DFF: (Synchronous)

```
module DFF(Rst, Clk, D, Q);
  input Rst, Clk, D;
  output Q;
  reg Q;
  always@(posedge Clk)
    if (Rst) Q=1'b0;
    else Q=D;
endmodule
```

Typical Design Styles of 1C1PD-FSM


A. Typical Finite State Machine

1. Manual Design: Reviewed and illustrated by a simple example.
2. Automatically Synthesis: Using Verilog HDL.

B. Algorithmic State Machine (ASM)

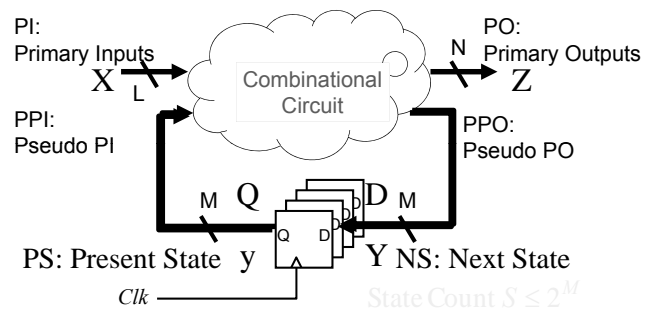C. Counter-Based Finite State Machine


Huffman Model for a Finite State Machine Single-Clock Single-Phase DFF Array-based



Switch-Case

case, casex, casez
 
```
case (expression)
  constant1: statement1;
  :
  constantj: statementj;
  :
  default: statementd;
endcase
```



```
casex (c)
  4'b00xx: statement1;
  :
  4'b0xxx: statementj;
  :
  default: statementd;
endcase
```

```
casez (c)
  8'b01z?11??: statement1;
  :
  8'b1100????: statementj;
  :
  default: statementd;
endcase
```


Typical Verilog Description

Example of Mealy Machine: A Lock with Password 1101

```
module Lock(Clk, X, Z)
input   Clk, X;
output  Z;
reg     Z;
parameter W1011=2'b00, W011=2'b01, W11=2'b10, W1=2'b11;
reg [1:0] Present_State, Next_State;
always@(posedge Clk)
  Present_State = Next_State;
always@(X or Present_State) begin
  Next_State = Present_State;
  case(Present_State)
    W1011 : Next_State = X ? W011 : W1011;
    W011  : Next_State = X ? W011 : W11;
    W11   : Next_State = X ? W1  : W1011;
    W1    : Next_State = X ? W011 : W11;
    default: Next_State = W011;
  endcase
endcase
end // always
endmodule
```


State Diagram

Example of Moore Machine: Recent Ones

 

State Diagram

Example of Moore Machine: Recent Ones

 

Typical Verilog Description

Example of Mealy Machine: A Lock with Password 1101

```
module Recent1s(Clk, X, Z)
input   Clk, X;
output  [1:0] Z;
reg     [1:0] Z;
reg [1:0] Present_State, Next_State;
always@(posedge Clk)
  Present_State = Next_State;
always@(X or Present_State) begin
  Next_State = Present_State;
  case(Present_State)
    0 : Next_State = X ? 1 : 0;
    1 : Next_State = X ? 2 : 1;
    2 : Next_State = X ? 1 : 0;
    3 : Next_State = X ? 2 : 1;
    default: Next_State = 0;
  endcase
endcase
end // always
assign Z = Present_State[1] + Present_State[0];
endmodule
```

Moore decoder from present state to output

Algorithmic State Machine

- A special design style of general finite state machines.
- It can be designed by mapping from the flow-chart.
- It can be synthesized manually.
- High area overhead and low performance due multiplexer stack.

1. Describe your system in pseudo code;
2. Draw the flow-chart;
3. Map the flow-chart to ASM chart;
4. Map the ASM chart to the HDL or circuit.

Pseudo Code

- A high-level, almost-executable description
- Used for leader's instruction, explanation of algorithms, etc.
- Pascal-like or C-like codes with some comprehensive English is preferable.
- Example:

```

1 C=alg()
2 {
3   C=init()
4   For each P, j, propagate C=propagate(j);
5   While( C!=done) do:
6     Get a gate g from C frontier that has the minimum delay;
7     j=propagate-g;
8     //containing value of g;
9     the control of g = PATT.PP;
10  Repeat:
11    Select an input of gate g, i, with a delay less N;
12    If find( g.i) then control(g) = SUCCESS;
13    Until control(g)=SUCCESS or no input less than N value;
14    If control(g)=FAILURE then propagate=C=propagate(g);
15  }
16  Insert value at P in the control pattern;
17 }
18 propagate=C=propagate(g)
19 {
20   For each gate FF from gate g, do of g
21   if a # PATT; NEXT; NEXT() as a done and have a done case
22   from propagate C=propagate(g);
23   else gate is into C frontier.


```

Basic Flowchart Elements


- Flow and Direction:
- Decision:
- Process:
- Terminals:
- (Card) Input:
- Specific Outputs:

Sequence Control if-then-else

if ($\diamond C$) { Y } else { N }

 

Sequence Control switch

 

```

if (expr==const1) {P1}
else if (expr==const2) {P2}
  else if (expr==const3) {P3}
  else if (expr==const4) {P4}
  else {Pdefault}


```

```

switch (expr) {
  case const1: {P1} break;
  case const2: {P2} break;
  case const3: {P3} break;
  case const4: {P4} break;
  ...
  default: {Pdefault}
}

```


Sequence Control For-loop

 


```

for(i=1; i<=9; i++) {
  for(j=1; j<=9; j++)
    printf("%dX%d=%2d\t", i, j, i*j);
  printf("\n");
}

```

 


 Sequence Control Do-While-Loop and While-Do-Loop



Map Flowchart to ASM Chart

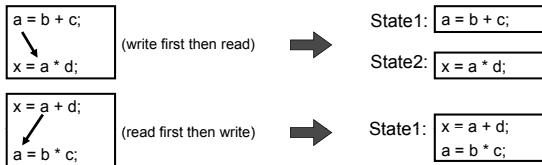- Split Processes in flowchart into States that each state can be executed in 1 clock cycle.
- Note that a WR-dependent process should be split into two states.



Map Decision to Demultiplexer

- If the condition is a 1-bit variable, directly map the decision to a demultiplexer that is a combinational gate (i.e., it takes a delay less than the clock cycle).




- The clock state of a decision is belong to the last process, therefore the last process should be split into 2 states if there is a WR-dependency.




Map Decision with Expression to Diamond

 
- If the condition is an expression instead of a direct input, map the decision to a diamond.
- A diamond is composed of a demultiplexer and an extra process.





- When the delay of combinational circuit $f()$ is too large, it is better to split it to two states with a demultiplexer.

 

Example 8-bit Multiplier

 

For Instance

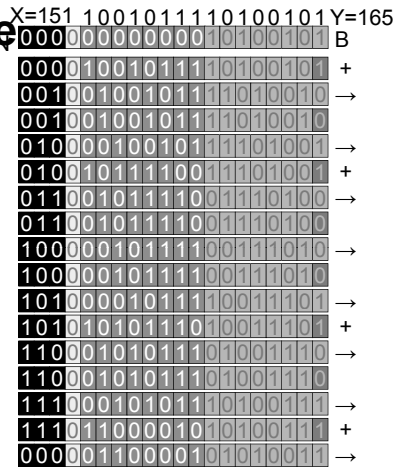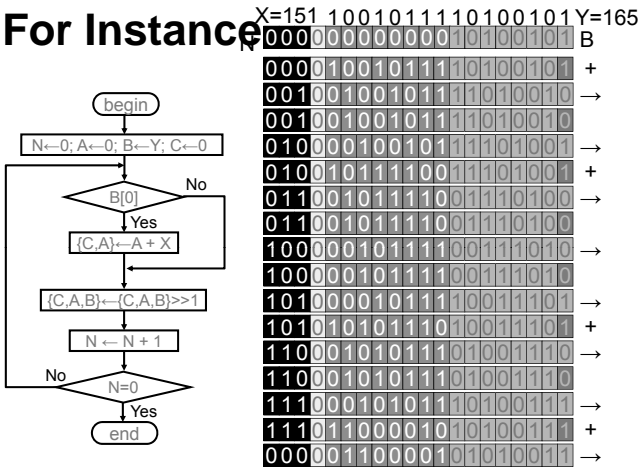

Example of Verification using C

```
#include <stdio.h>
main()
{
    unsigned char X, Y, C, A, B, N, Verified;
    int i, P, Q, Acc, S;

    Verified = 1;
    for(i=0; i < (1<<16); i++) {
        X=i/(1<<8);
        Y=i%(1<<8);
        P=X*Y; // Golden Circuit

        // Algorithm Started Here
        N=0; A=0; B=Y; C=0; // Initialization
        do {
            // Accumulate
            if(B&2) {Acc = A + C*256 + X; A=Acc%256; C=(Acc>>8)%2;}
            // Shift CAB
            S = C*65536 + A*256 + B; S = S >> 1; B=S%256; A=(S>>8)%256; C=(S>>16)%2;
            N++;
        } while (N!=8);
        Q=(A<<8)+B;
        if(Q!=P) {
            Verified=0;
            printf("Error when X=%d, Y=%d, Q=%d\n", X, Y, Q);
            break;
        }
    }
    if(Verified) printf("The circuit is exhaustively functionally verified.\n");
}
```


Example: Verification using Assembly Language

```


BEGIN:    MOV     N, #States
          CLR     A
          CLR     C
LOOP:     MOV     B, X
          JE      SHIFT
          ADC     Y
SHIFT:    SHR     CAB
          DEC     N
          JNZ    LOOP
          END
    
```

C and Assembly codes can be the fast logic simulator.


Example: 8-bit Multiplier

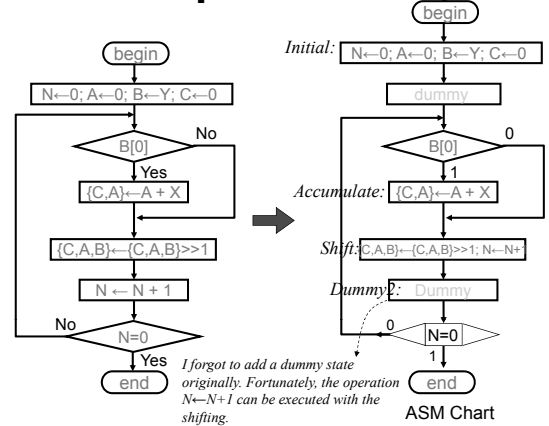



Map ASM Elements to Sequencer

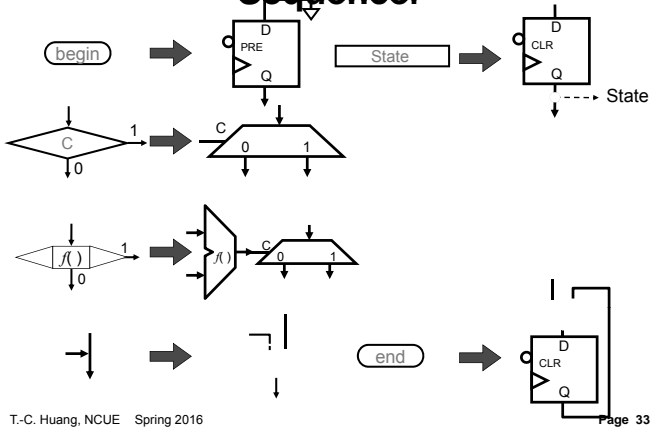

Map to State Sequencer

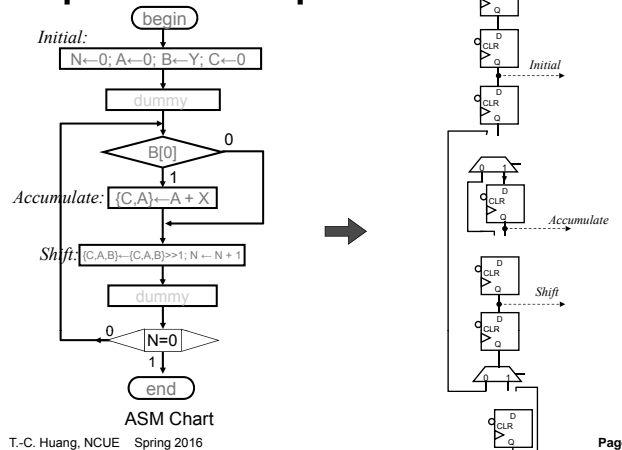


Map to ALU

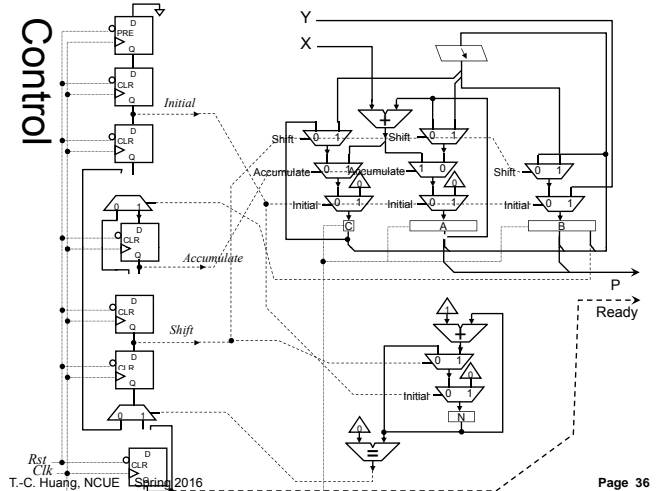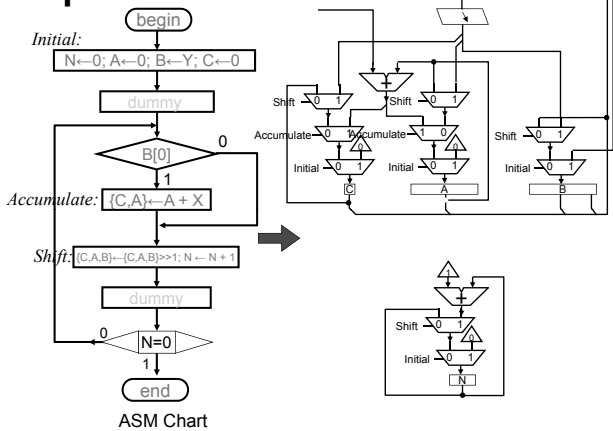

N-Bit Multiplier

assign P = A * B;

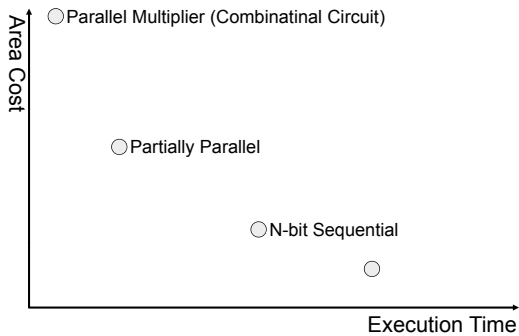

Counter/Timer Based State Machine

Counters in General Sense

◆ A general counter is an FSM that NS depends only on PS.

➤ Binary Counter

- Ripple Counter: Toggle FFs triggered by Input.
- Parallel counter takes much space while FSM design takes much time.

➤ Gray Counter

- Minimum transition count for low power, low noise application

➤ Shifting Counter

- Incomplete coding.
- Almost zero propagation time in Huffman model of sequential circuits → Fastest

• Examples:

➤ Ring Counter

- 1-hot code for some direct or fast application

➤ Johnson Counter

- Fastest and with 2N states

➤ LFSR (Random) Counter

- Random number generation, random test and compression
- Decoder required for use as counter.


Example: Counters

➤ Basic Up-Counting Counter:

```
module DFF(Clk, Q);
input Clk;
output [7:0] Q;
reg [7:0] Q;
always@(posedge Clk)
    Q=Q+1;
endmodule
```

➤ Resettable Counter:


(Asynchronous)

 

```
module DFF(Rst, Clk, Q);
input Rst, Clk;
output [15:0] Q;
reg [15:0] Q;
always@(posedge Clk or posedge Rst)
    if(Rst) Q=15'b0;
    else Q=Q+1;
endmodule
```

➤ Resettable Counter:

(Synchronous)

 

```
module DFF(Rst, Clk, Q);
input Rst, Clk;
output [31:0] Q;
reg [31:0] Q;
always@(posedge Clk)
    if(Rst) Q=31'b0;
    else Q=Q+1;
endmodule
```

Example: Counters

➤ Basic Down-Counting Counter:

```
module DFF(Clk, Q);
input Clk;
output [7:0] Q;
reg [7:0] Q;
always@(posedge Clk)
    Q=Q-1;
endmodule
```

➤ Loadable Counter:

```
module DFF(Load, Clk, D, Q);
input Load, Clk, D;
output [15:0] Q;
reg [15:0] Q;
always@(posedge Clk)
    if(Load) Q=D;
    else Q=Q+1;
endmodule
```

➤ Modulo Counter:

```
module DFF(Rst, Clk, Q);
input Rst, Clk;
output [7:0] Q;
reg [7:0] Q;
always@(posedge Clk)
    if(Rst) Q=7'b0;
    else if(Q==99) Q=7'b0; // %100
    else Q=Q+1;
endmodule
```

Counter/Timer Based State Machine

Combination of Counter and FSM

