


VLSI Design

Tsung-Chu Huang

Department of Electronic Engineering
National Changhua University of Education
Email: tch@cc.ncue.edu.tw

2016/03/01

Syllabus Structure Bottom-up Hierarchy

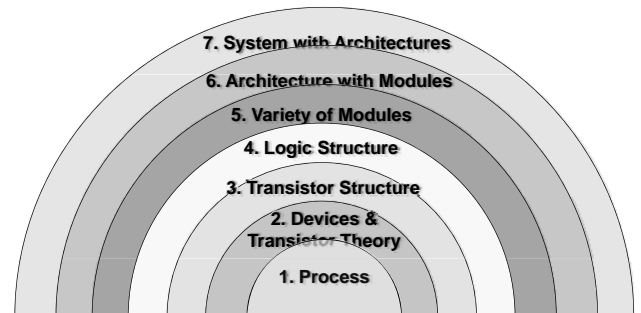


Transistor Power/Timing Models Summary

- Switch Models
 - ✓ Ideal Switch: Functional simulation without timing
 - ✓ Resistive Switch: Static power evaluation
 - ✓ Capacitive Switch: Dynamic power evaluation
 - ✓ RC Switch: Basic power and timing evaluation
- Transistor Structure Model
 - ✓ El More Model: loop RC additive.
 - ✓ Rabaey Model: Logical and branch efforts
- IDS Models
 - ✓ Shockley First-Order Equation: accurate manual derivation
 - ✓ Sub-threshold Models
- SPICE Models
 - ✓ Complicate Simulation

Transistor Network Relay Logics


- Stack Effect
 - ✓ Parallel Switch: $S_{on} = A_{on} + B_{on}$, $R_s = R_A // R_B$
 - ✓ Serial Switch: $S_{on} = A_{on} \cdot B_{on}$, $R_s = R_A + R_B$
 - ✓ Parallel Capacitors: $C = C_A + C_B$
- Body Effect
 - ✓ is the threshold voltage changing of source-bulk voltage due to transistor connection in series.
 
$$V_{t2} \approx V_{t1} + 0.6\sqrt{V_{D1}}$$




Logic Completeness and Switch

 
1. {And, Or, Not} is a complete logic set.
2. A logic set is complete if and only if it can combine to all functions of another complete logic set, such as {NAND} and {NOR}
3. A basic relay (switch) logic can represent either AND or OR function only.
4. Example: $F = A(B+C)+D$



Transmission Gate

 

Tri-State

 


High Impedance
Floating (connection)
Hi-Z
'z'

Tri-State Logic


AND	0	Z	1	OR	0	Z	1
0	0	0	0	0	0	Z	1
Z	0	Z	Z	Z	Z	Z	1
1	0	Z	1	1	1	1	1

CMOS Logic

 


1. N network is a relay logic of $\overline{F(X)}$
 2. P network is a relay logic of $F(\overline{X})$
- AND \longleftrightarrow OR

Transfer Function of CMOS Inverters

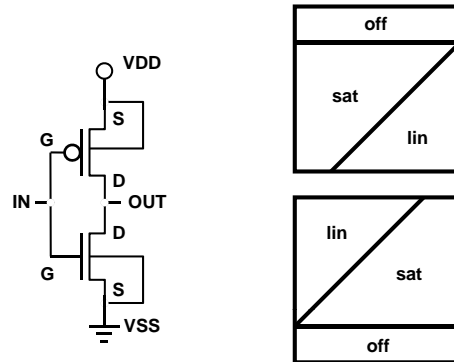

Transfer Function of CMOS Inverters

 


Transfer Function of CMOS Inverters

$$\text{Inverter Size} = S = \frac{\beta_n}{\beta_p} = \frac{\mu_n W_n L_p}{\mu_p L_n W_p} \approx 2.6 \frac{W_n L_p}{L_n W_p}$$

$$\text{Inversion Voltage: } = V_{inv} = \frac{V_{DD} + V_{tp} + V_{tn} \sqrt{S}}{1 + \sqrt{S}}$$

$$\text{Unit-size \& Equal-inversion: } V_{inv} = \frac{V_{DD}}{2}$$

Beta-Ratio Effects

 

Unary-Sized Inverter


Inverter Size = S =

$$\frac{\beta_n}{\beta_p} \approx 2.6 \frac{W_n L_p}{L_n W_p}$$

When $L_p=L_n=L$,



$$W_p:W_n \approx 2.6:1 \approx 2$$

PS. Usual Layout Skill:

 



Min.-Size: $L=L_{min}$, $W=W_{min}$

Identical Inverter Cascade

  



Usually, the input range is limited to the points with a slope 45 degrees.

Noise Margin

  








Butterfly Chart

Representing Static Noise Margins

  


SNMs Everywhere !

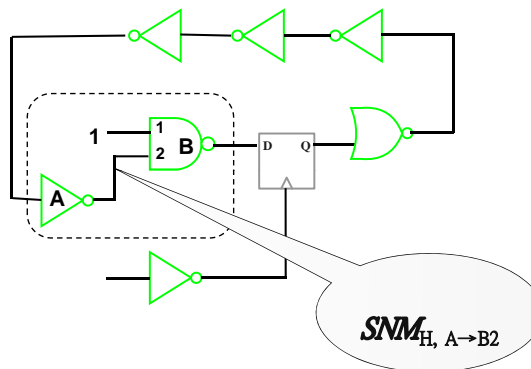

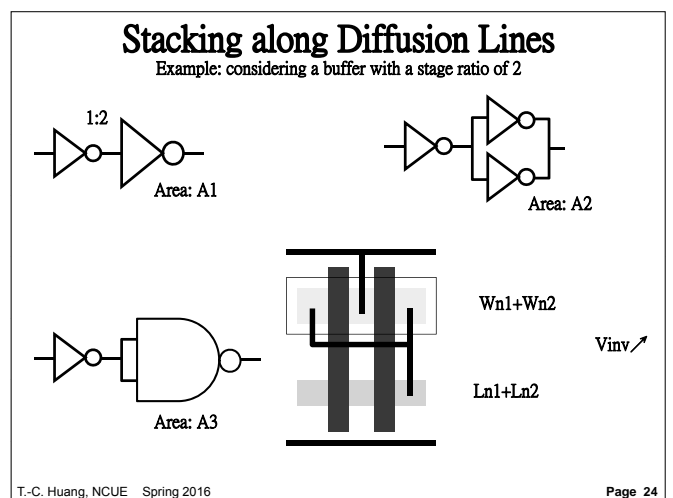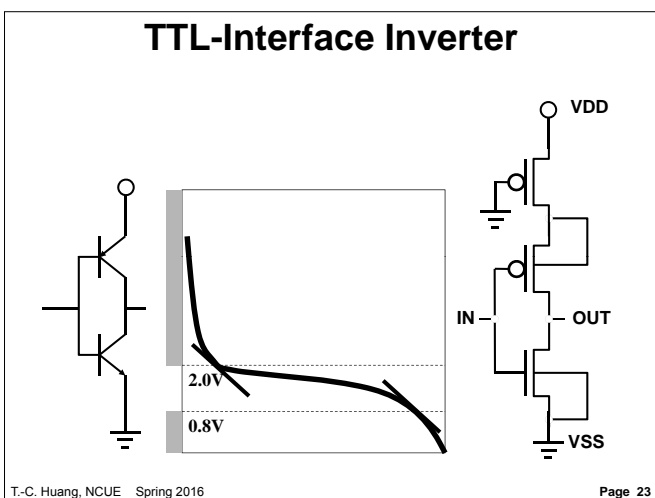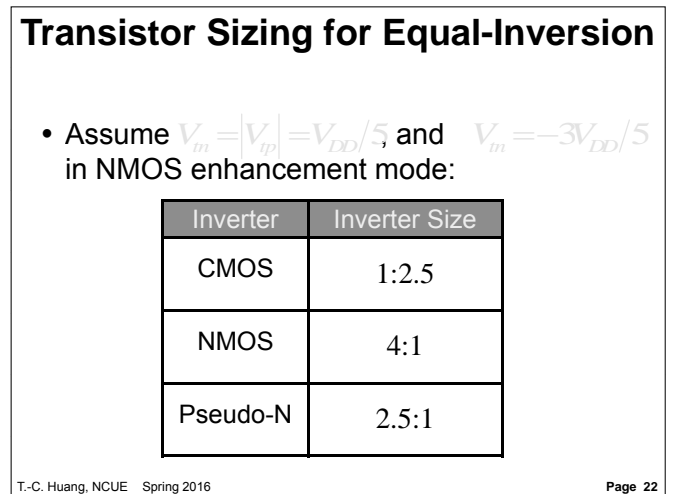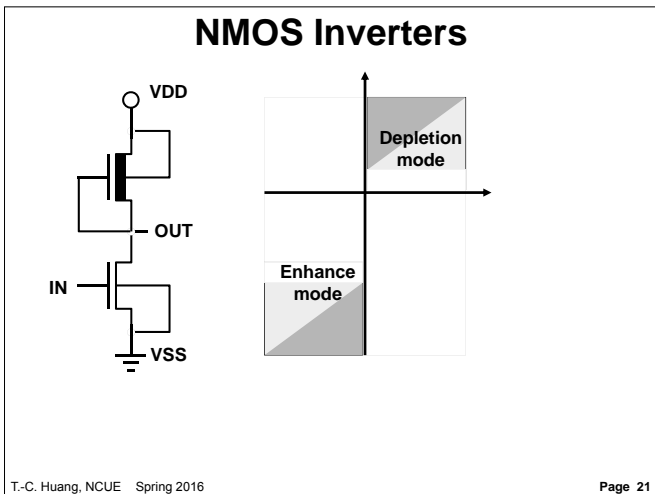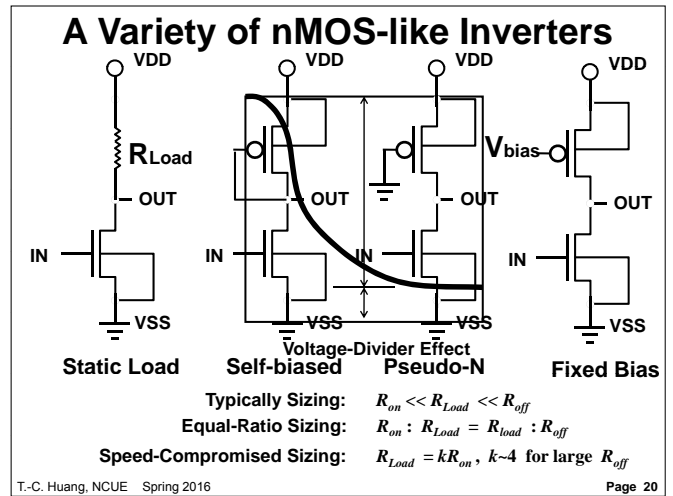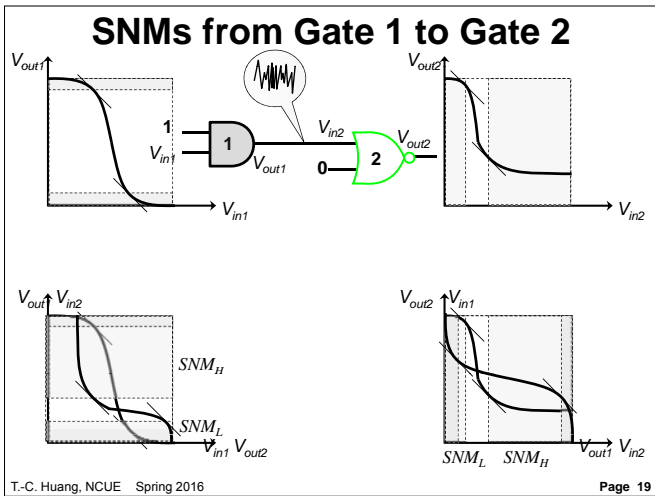

Myth: 180° Oscillator?

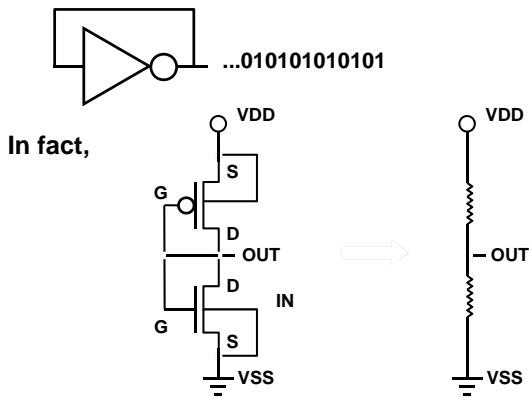


Stick Diagram


1. Representations of Layout

- Grid-base graph
- EDIF: hierarchical language with coordinates.
- Stick diagram: for sketch or plan


2. Example :

 

2-to-1 Multiplexer

 

TG-based Multiplexer

 


Bidirectional
No tri-state in ideal timing
Bus Contention possibly !

Example : $F = \overline{(A+B)(C+D)}$



$$F = \bar{A}\bar{B} + \bar{C}\bar{D}$$

P network :

 


$$\bar{F} = (A+B)(C+D)$$

N network :

  


Euler Path

 
1. Topology in 18th Century Applied in CMOS
2. N path: Relay logic of N network
3. P path: Relay logic of P network
4. N path crosses p path at input X and \bar{X} .




Euler Path Guided Layout

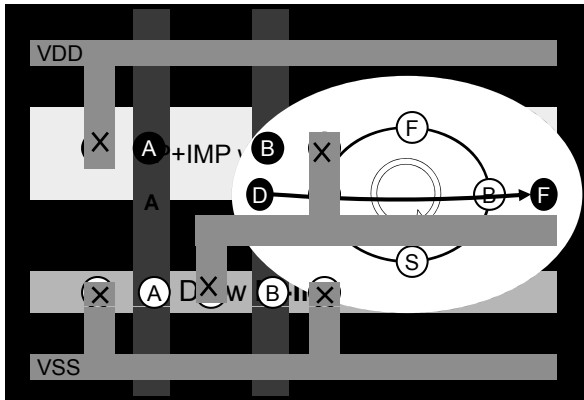


Example : $F = \overline{(A+B)}(C+D)$

 

Cell-Based Channel Routing

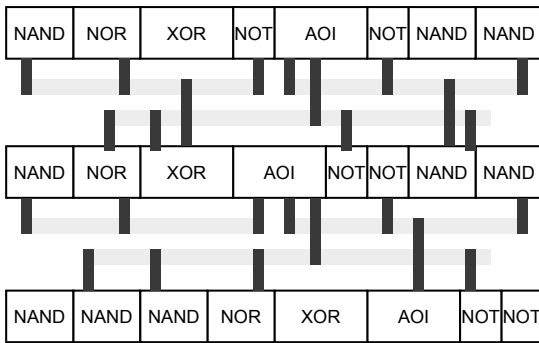


Channel Routing

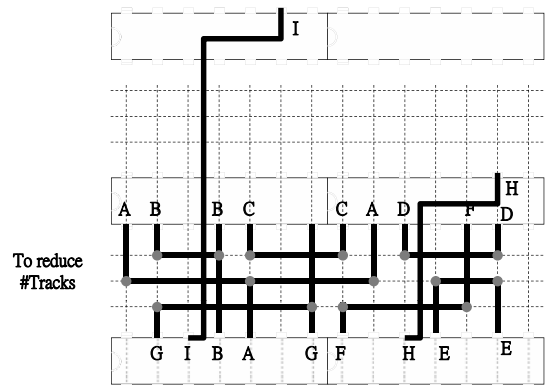

LEA: Left-Edge Algorithm

 
1. Sort by length
2. Select from Left Edge




Primitive Gates

1. Primitive: A-tomic (Cannot be cut off)
2. Properties of a CMOS Primitives:
 - Either pulled up or pulled down;
 - Current from or to the single output
 - $IDDQ=0$ for Ideal CMOS
3. Usual Symbols:
 - directly assembled without wire.
 - {AND, OR} Combo ended with an Inverter

Complex Primitive Trivial Example

 


Usual Example and Naming

 


OAI231

Interlaces of Diffusion Lines

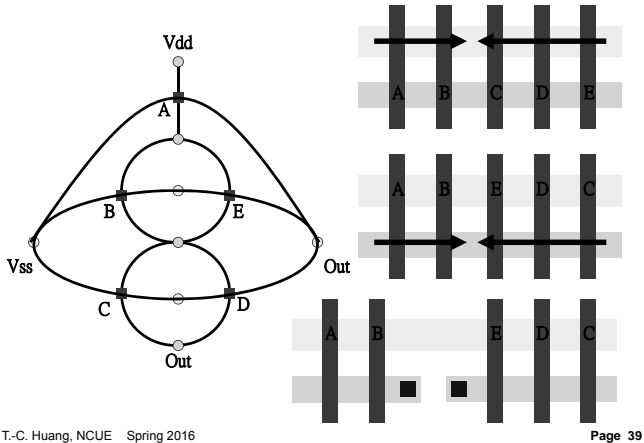


Minimum Interlace Algorithm

Example: $Out = (A+B)(C+D)+EF$

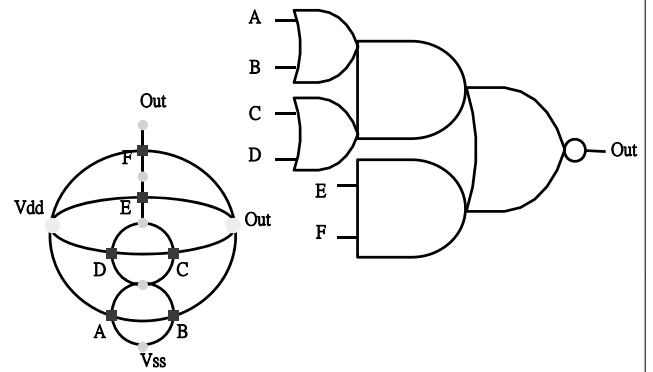


Minimum Interlace Algorithm

 - Adding a pseudo input to each sub-gate such that each sub-gate has odd inputs.




Minimum Interlace Algorithm

 - Rotate each axis to reduce the inner interlaces




Output Capacitance Minimization

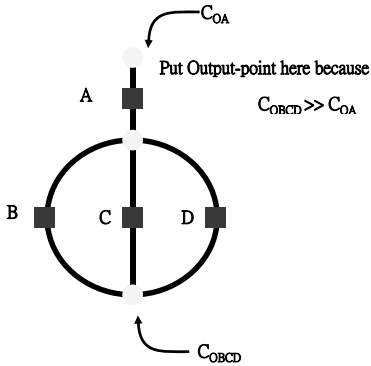


Memory – Latches and Registers

 - Prior to '90s, they're used to be confused.
- Latch: Level Sensitive
- 50's Flipflop (Very slow frequency):




 - Later Flipflop: Edge Triggered
- Register: Loadable or Hold




Static Gate Based Latch Example: Resettable D Latch

Switch-Based Static Latch and Flipflop

 


Tri-state Inverter

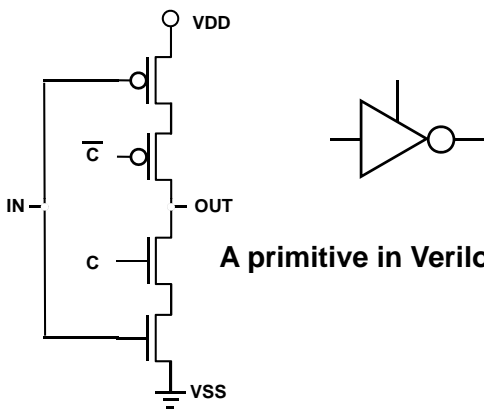


A primitive in Verilog: notif1

Basic Concept on BiCMOS Inverters

 - Compared with Bipolar Logics:
 - CMOS Logics: Low power ($I_{DDQ} \rightarrow 0$)
 - Poor drive capability
- Basic idea of BiCMOS Inverter:



BiCMOS Inverter

 

Transistor Sizing & Reordering

- Minimizing Area
- Maximizing/Equalizing Noise Margin
- Minimizing/Equalizing Rising & Falling Time
- Minimizing Propagation Time
- Minimizing Power Dissipation
- Reducing Glitch
- Minimizing Charge Sharing Effect
- Increasing Regularity for EDA

Roughly Area Estimation

- In several synthesis tools (2000):
An N-input CMOS Primitive Cell:
($0.5+0.5N$) units (compared to a unit inverter)
- Dependent on Layout Style

NMOS Logic Array

