




VLSI Design

Tsung-Chu Huang

Department of Electronic Engineering
National Changhua University of Education
Email: tch@cc.ncue.edu.tw

2016/04/19

Basic Model of a MOSFET

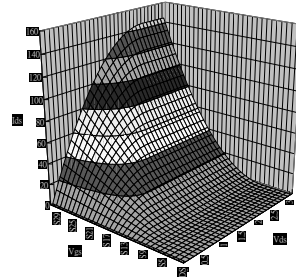

Saturation region:

$$I_{ds} = K \frac{W}{L} \frac{(V_{gs} - V_t)^2}{2}$$


Linear region:

$$I_{ds} = K \frac{W}{L} [(V_{gs} - V_t)V_{ds} - \frac{V_{ds}^2}{2}]$$


For recent micron tech:

$$K_n \approx 2.5K_p \approx 100 \mu A$$


$$V_t \approx 0.5V$$

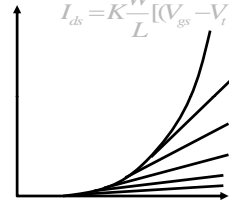

A 10T+C 2-Stage Simple OP AMP

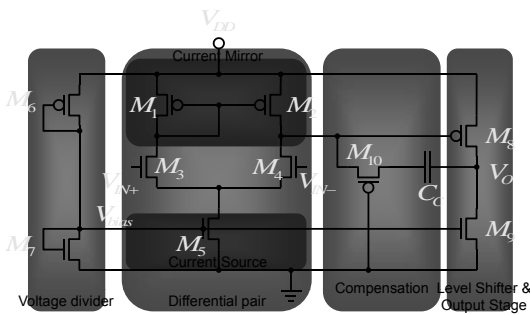

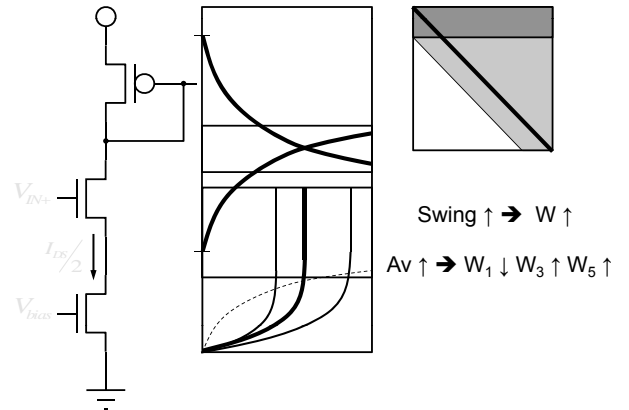
Half Operational Trans-conductance Amplifier




Swing $\uparrow \rightarrow W \uparrow$

$A_v \uparrow \rightarrow W_1 \downarrow W_3 \uparrow W_5 \uparrow$

Voltage-Divider Biasing Circuit

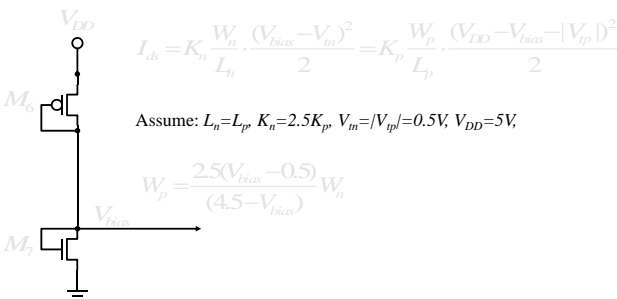

Differential Amplifier (Simple OTA)

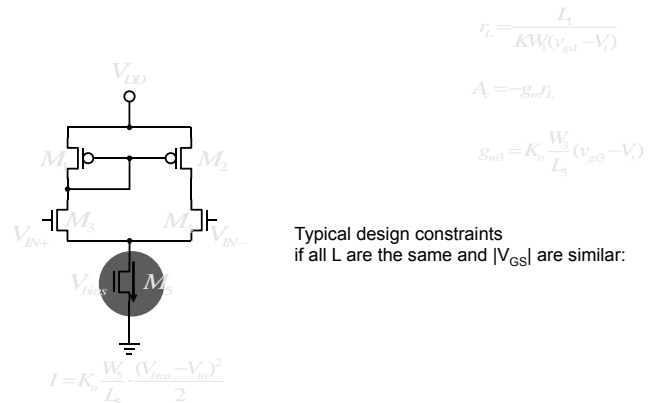


Simulation – Differential Amplifier (1)

```


Differential Amplifier
.lib 'mm0355v1' tt
.global dd
Vdd dd 0 5
.param biasing = 2
Mp1 g 0 dd dd pch L=0.35u W=2.5u
Mp2 o 0 dd dd pch L=0.35u W=2.5u
Mn3 g in+ m m nch L=0.35u W=1u
Mn4 o in- m m nch L=0.35u W=1u
Mn5 m bias 0 0 nch L=0.35u W=1u
Vbias bias 0 biasing
VIN1 IN1 0 2.5
VIN2 IN2 0 2.5
Vin+ in+ IN1 AC 1
Vin- in- IN2 0
.AC DEC 101 1 100G SWEEP biasing LIN / 1 1
.plot
.options post
.end
    
```

1. Sweeping selected parameters
2. Optimization
3. Alter
4. C Sscript

Simulation – Differential Amplifier (2)

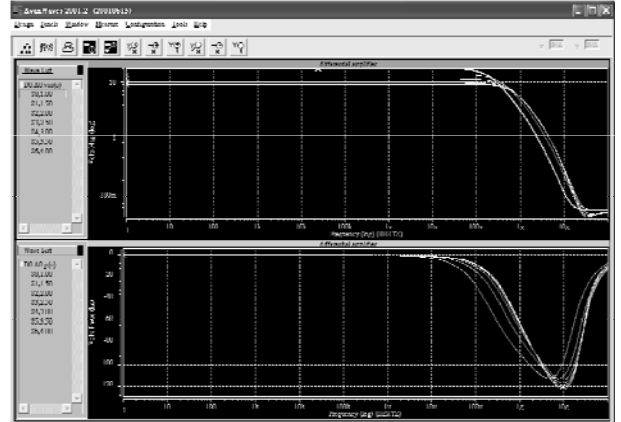

Level Shifter & Driver

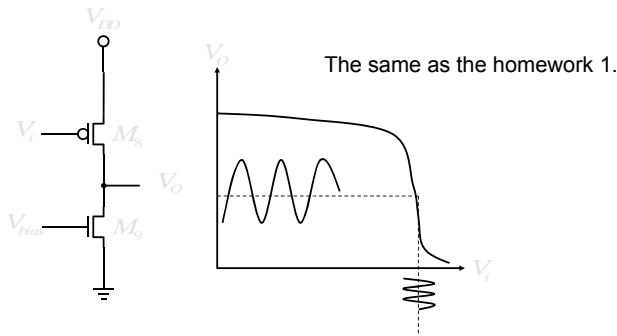

Operating Points

Add .OP operating-point analysis

```

Differential Amplifier
.lib 'mm0355v1' tt
.global dd
Vdd dd 0 5
Mp1 g 0 dd dd pch L=0.35u W=2.5u
Mp2 o 0 dd dd pch L=0.35u W=2.5u
Mn3 g in+ m m nch L=0.35u W=1u
Mn4 o in- m m nch L=0.35u W=1u
Mn5 m bias 0 0 nch L=0.35u W=1u
Mp6 bias bias dd dd pch L=0.35u W=2.5u
Mp7 bias bias 0 0 nch L=0.35u W=2.5u
VIN1 IN1 0 2.5
VIN2 IN2 0 2.5
Vin+ in+ IN1 AC 1
Vin- in- IN2 0
.AC DEC 101 1 10G
.options post
.OP
.end
    
```

```

**** operating point status is all simulation time is 0.
node =voltage node =voltage node =voltage
+0:bias = 1.3476 0:dd = 5.0000 0:g = 3.6991
+U:in+ = 2.5000 0:in- = 2.5000 0:in1 = 2.5000
+0:in2 = 2.5000 0:m = 1.4520 0:o = 3.6991
    
```

Example


A 9T Non-Compensated OPAMP Design

```


Operational Amplifier
.lib 'mm0355v1' tt
.global dd
Vdd dd 0 5
Mp1 g g dd dd pch L=0.35u W=2.5u
Mp2 o g dd dd pch L=0.35u W=2.5u
Mn3 g in+ m m nch L=0.35u W=1u
Mn4 o in- m m nch L=0.35u W=1u
Mn5 m bias 0 0 nch L=0.35u W=1u
Mp6 bias bias dd dd pch L=0.35u W=1u
Mn7 bias bias 0 0 nch L=0.35u W=2.5u
Mp8 out o dd dd pch L=0.35u W=4u
Mn9 out bias 0 0 nch L=0.35u W=1u
VIN1 IN1 0 2.5
VIN2 IN2 0 2.5
Vin+ in+ IN1 AC 1
Vin- in- IN2 0
.AC DEC 101 1 100G
.options post
.end
    
```

Example

A 9T OPAMP Design

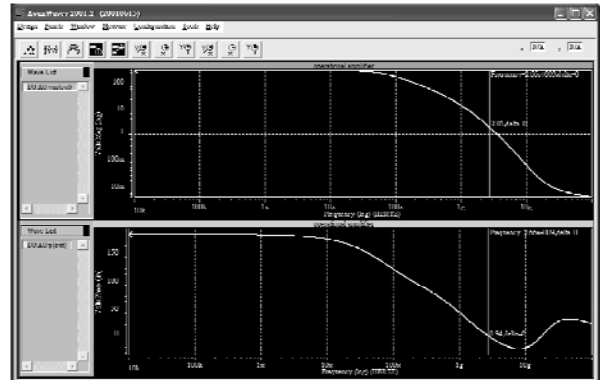


Basic Negative Feedback System

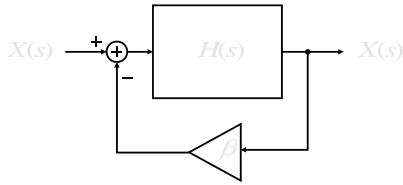

Close loop transfer function: $T(s) = \frac{H(s)}{1 + \beta H(s)}$

Barkhausen's criteria: $|\beta H| \leq 1 @ \angle \beta H = -180^\circ \Rightarrow \text{Stable}$

Typical Compensation on Bode Plot

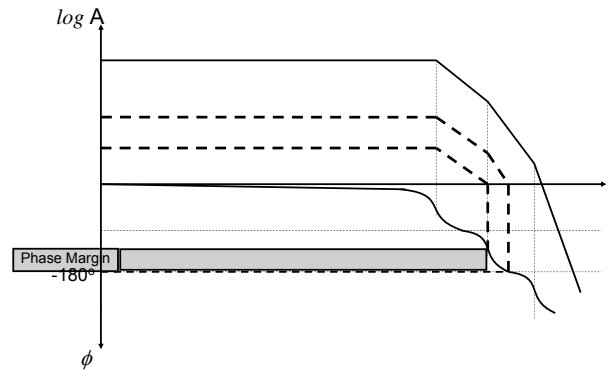


Typical Frequency Compensation

1. Dominant-Pole Compensation
2. Pole-Zero Compensation
3. Miller Compensation (Pole-Splitting)

Miller Compensation

A 9T+C OPAMP

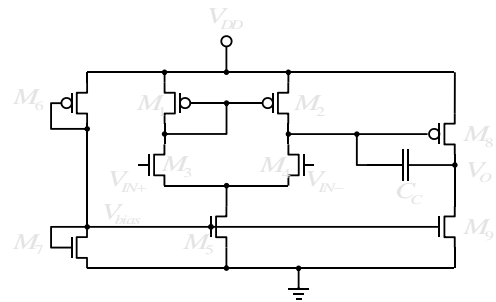


Miller Compensation

A 9T+C OPAMP

```
Operational Amplifier
.lib 'mm0355v1' tt
.global dd
.param Cap = 0
Vdd dd 0 5
Mp1 g g dd dd pch L=0.35u W=2.5u
Mp2 o g dd dd pch L=0.35u W=2.5u
Mn3 g in+ m m nch L=0.35u W=1u
Mn4 o in- m m nch L=0.35u W=1u
Mn5 m bias 0 0 nch L=0.35u W=1u
Mp6 bias bias dd dd pch L=0.35u W=1u
Mn7 bias bias 0 0 nch L=0.35u W=2.5u
Mp8 out o dd dd pch L=0.35u W=4u
Mn9 out bias 0 0 nch L=0.35u W=1u
Cc out o Cap
VIN1 IN1 0 2.5
VIN2 IN2 0 2.5
Vin+ in+ IN1 AC 1
Vin- in- IN2 0
.AC DEC 101 10K 100G SWEEP Cap DEC 2 1f 100p
.options post
.end
```

Miller Compensation


A 9T+C OPAMP

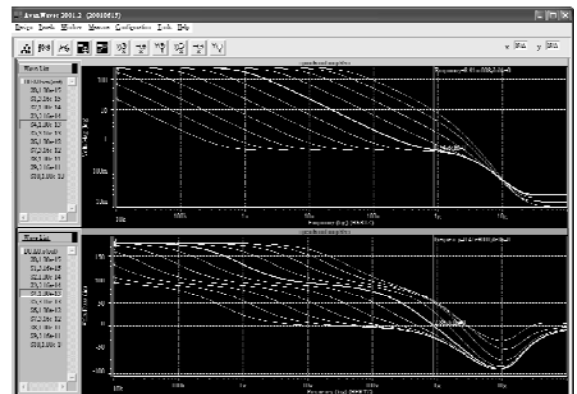

Cross-Match Floor-Planning (1)

Basic Matching:


MP1	g	g	dd	dd	pch	L=0.35u	W=2.5u
MP2	o	g	dd	dd	pch	L=0.35u	W=2.5u

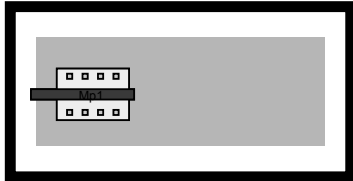

Cross-Match Floor-Planning (2)

Cross Matching:

MP1	g	g	dd	dd	pch	L=0.35u	W=1.25u	M=2
MP2	o	g	dd	dd	pch	L=0.35u	W=1.25u	M=2

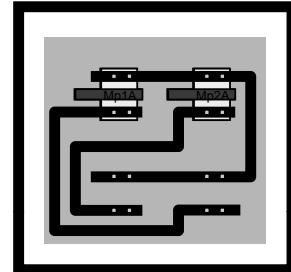

Cross-Match Floor-Planning (3)

An Example for Coarse Floor-planning:

