

VLSI Design

Tsung-Chu Huang

Department of Electronic Engineering
National Changhua University of Education
Email: tch@cc.ncue.edu.tw

2011/11/28

T-C. Huang, NCUE Fall 2011

Page 1

Basic Model of a MOSFET

Saturation region:

$$I_{ds} = K \frac{W}{L} \cdot \frac{(V_{gs} - V_t)^2}{2}$$

Linear region:

$$I_{ds} = K \frac{W}{L} [(V_{gs} - V_t)V_{ds} - \frac{V_{ds}^2}{2}]$$

For recent micron tech:


$$K_n \approx 2.5K_p \approx 100\mu A$$

$$V_t \approx 0.5V$$

T-C. Huang, NCUE Fall 2011

Page 2


A 10T+C 2-Stage Simple OP AMP

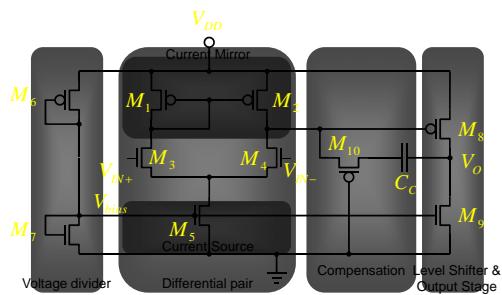

T-C. Huang, NCUE Fall 2011

Page 3

Voltage-Divider Biasing Circuit

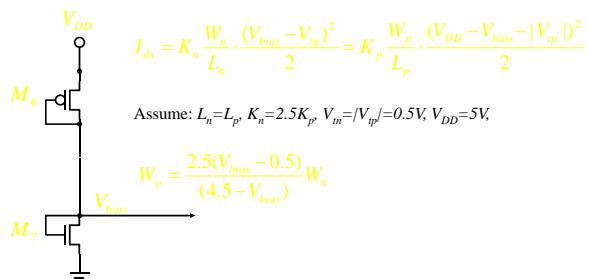

T-C. Huang, NCUE Fall 2011

Page 4


Differential Amplifier (Simple OTA)

$$r_i = \frac{L_s}{K W_l (V_{gs1} - V_t)}$$

$$A_v = -g_m r_i$$

$$g_{m3} = K_n \frac{W_3}{L_3} (V_{gs3} - V_t)$$


Typical design constraints
if all L are the same and $|V_{GS}|$ are similar:

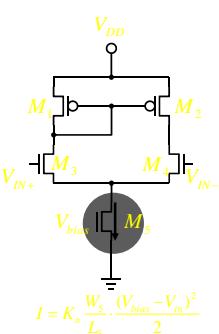

T-C. Huang, NCUE Fall 2011

Page 5

Simulation – Differential Amplifier (1)

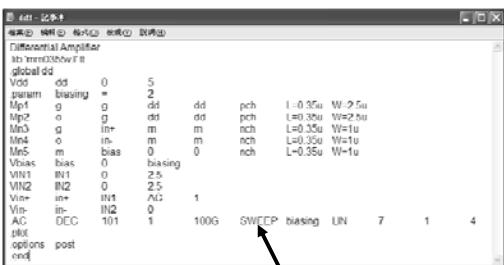


1. Sweeping selected parameters
2. Optimization
3. Alter
4. C Script

T-C. Huang, NCUE Fall 2011

Page 6


Simulation – Differential Amplifier (2)

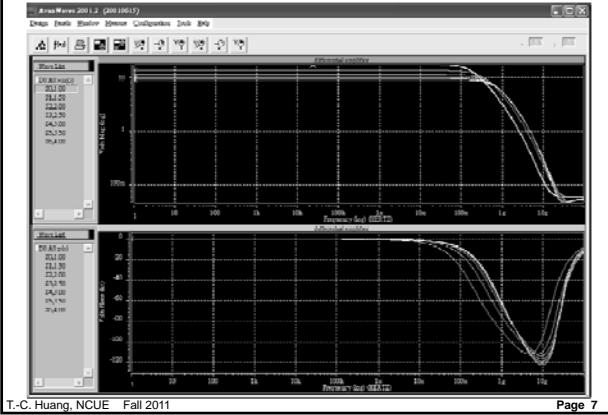

T-C Huang, NCUE Fall 2011

Page 7

Level Shifter & Driver

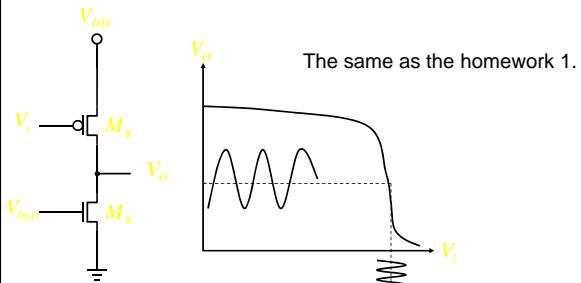

The same as the homework 1.

T-C Huang, NCUE Fall 2011

Page 8

Operating Points

Add .OP operating-point analysis

```
Differential Amplifier
.lib 'mm0355v.1' tt
.global dd
Vdd dd 0 5
Mp1 g g dd dd pch L=0.35u W=2.5u
Mp2 o g dd dd pch L=0.35u W=2.5u
Mn3 g in+ m m nch L=0.35u W=lu
Mn4 o in- m m nch L=0.35u W=lu
Mn5 m bias 0 0 nch L=0.35u W=lu
Mp6 bias bias dd dd pch L=0.35u W=lu
Mn7 bias bias 0 0 nch L=0.35u W=2.5u

VIN1 IN1 0 2.5
VIN2 IN2 0 2.5
Vin+ in+ IN1 AC 1
Vin- in- IN2 0
.AC DEC 101 1 10G
.options post
.OP
.end

***** operating point status is all simulation time is 0.
node =voltage node =voltage node =voltage
+0:bias = 1.3476 0:dd = 5.0000 0:g = 3.6991
+v:in+ = 2.5000 0:in- = 2.5000 0:inl = 2.5000
+0:in2 = 2.5000 0:m = 1.4520 0:o = 3.6991
```

T-C Huang, NCUE Fall 2011

Page 9

Example

A 9T Non-Compensated OPAMP Design

```
Operational Amplifier
.lib 'mm0355v.1' tt
.global dd
Vdd dd 0 5
Mp1 g g dd dd pch L=0.35u W=2.5u
Mp2 o g dd dd pch L=0.35u W=2.5u
Mn3 g in+ m m nch L=0.35u W=lu
Mn4 o in- m m nch L=0.35u W=lu
Mn5 m bias 0 0 nch L=0.35u W=lu
Mp6 bias bias dd dd pch L=0.35u W=lu
Mn7 bias bias 0 0 nch L=0.35u W=2.5u
Mp8 out o dd dd pch L=0.35u W=4u
Mn9 out bias 0 0 nch L=0.35u W=lu


VIN1 IN1 0 2.5
VIN2 IN2 0 2.5
Vin+ in+ IN1 AC 1
Vin- in- IN2 0
.AC DEC 101 1 100G
.options post
.end
```

T-C Huang, NCUE Fall 2011

Page 10

Example


A 9T OPAMP Design

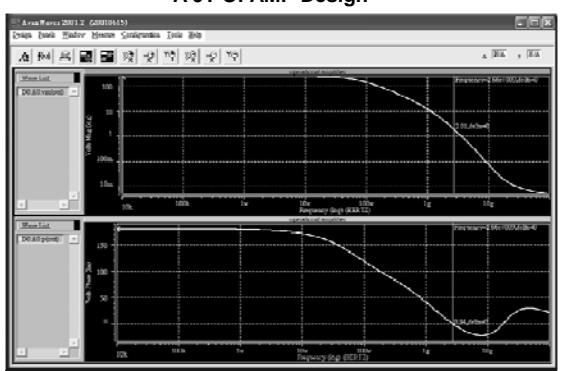

T-C Huang, NCUE Fall 2011

Page 11

Basic Negative Feedback System

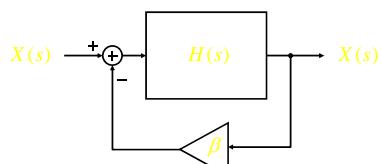


$$\text{Close loop transfer function: } T(s) = \frac{H(s)}{1 + \beta H(s)}$$

Barkhausen's criteria: $|\beta H| \leq 1 @ \angle \beta H = -180^\circ \Rightarrow \text{Stable}$

T-C Huang, NCUE Fall 2011

Page 12

Typical Compensation on Bode Plot

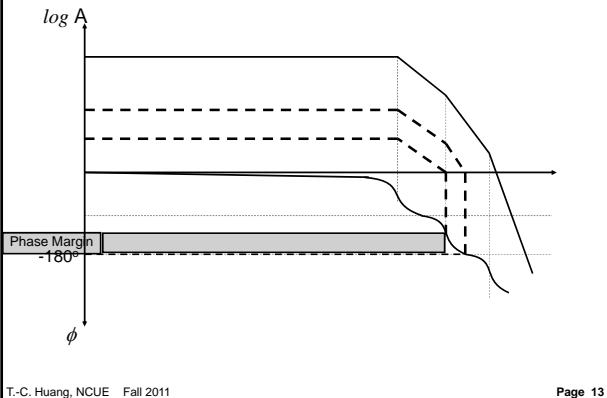

Typical Frequency Compensation


1. Dominant-Pole Compensation
2. Pole-Zero Compensation
3. Miller Compensation (Pole-Splitting)

T-C Huang, NCUE Fall 2011

Page 14

Miller Compensation

A 9T+C OPAMP

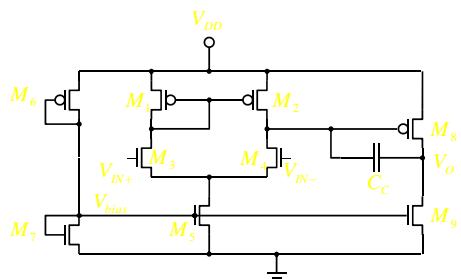

Miller Compensation

A 9T+C OPAMP


```
Operational Amplifier
.lib mm0355v.1' tt
.global dd Cap = 0
.param Cap = 0
Vdd dd 5
Mp1 g g dd dd pch L=0.35u W=2.5u
Mp2 o g dd dd pch L=0.35u W=2.5u
Mn3 g in+ m m nch L=0.35u W=1u
Mn4 o in- m m nch L=0.35u W=1u
Mn5 m bias 0 0 nch L=0.35u W=1u
Mp6 bias bias dd dd pch L=0.35u W=1u
Mn7 bias bias 0 0 nch L=0.35u W=2.5u
Mp8 out o dd dd pch L=0.35u W=4u
Mn9 out bias 0 0 nch L=0.35u W=1u
Cc out o Cap L=0.35u W=1u
VIN1 IN1 0 2.5
VIN2 IN2 0 2.5
Vin+ in+ IN1 AC 1
Vin- in- IN2 0
.AC DEC 101 10K 100G SWEEP Cap DEC 2 lf 100p
.options post
.end
```

T-C Huang, NCUE Fall 2011

Page 16

Miller Compensation


A 9T+C OPAMP

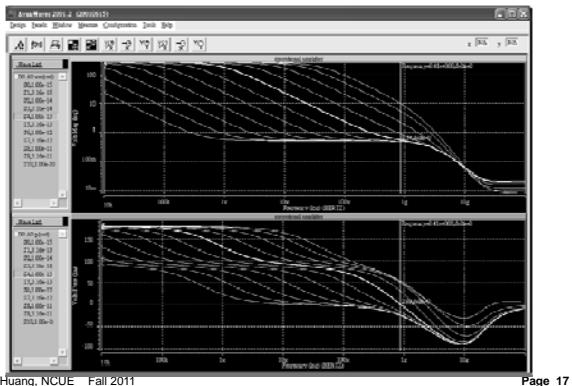

Cross-Match Floor-Planning (1)

Basic Matching:
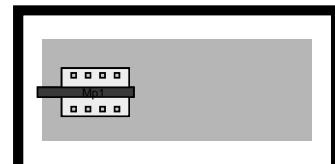
```
Mp1 g g dd dd pch L=0.35u W=2.5u
Mp2 o g dd dd pch L=0.35u W=2.5u
```




T-C Huang, NCUE Fall 2011

Page 18

Cross-Match Floor-Planning (2)

Cross Matching:

Mp1	g	g	dd	dd	pch	L=0.35u	W=1.25u	M=2
Mp2	o	g	dd	dd	pch	L=0.35u	W=1.25u	M=2

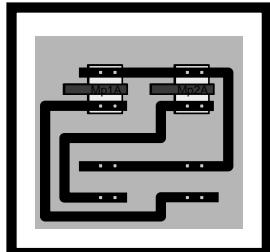


T.-C. Huang, NCUE Fall 2011

Page 19

Cross-Match Floor-Planning (3)

An Example for Coarse Floor-planning:

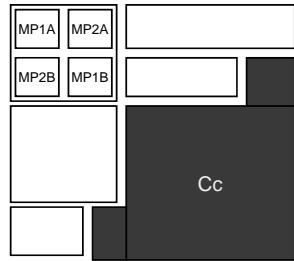

T.-C. Huang, NCUE Fall 2011

Page 20