


VLSI Design

Tsung-Chu Huang

Department of Electronic Engineering
National Changhua University of Education
Email: tch@cc.ncue.edu.tw

2011/11/21

Types of Logic ICs

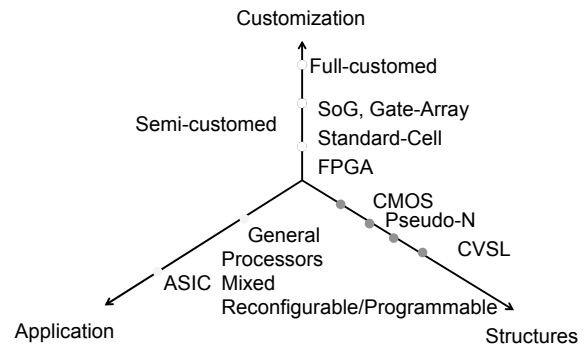

Transistor-Level Structure Outline

1. CMOS Logic Gate Design
2. Standard Cell Layout & Channel Routing
3. Gate Array Layout
4. Sea of Gates
5. CMOS Layout Guideline
6. Transmission Gate Layout
7. MUX Layout
8. Pass-Transistor Logic


Transistor-Level Structure Outline

1. CMOS Logic Gate Design
2. Standard Cell Layout & Channel Routing
3. Gate Array Layout
4. Sea of Gates
5. CMOS Layout Guideline
6. Transmission Gate Layout
7. MUX Layout
8. Pass-Transistor Logic

Rapid Prototyping


1. Prototyping: $Q \ll Q_{\text{product}}$ for test, debug, verification.
2. Rapid Prototyping: $t(Q) \ll t(Q_{\text{product}})$
3. Usual Rapid Prototyping wrt. Full Custom
 - Semi-Custom: saving the prior processes
 - Weinberger Array, Gate Array, SOG, e.t.c.
 - Standard-Cell: saving
 - PLD
 - 1) SPLD
 - 2) CPLD
 - 3) FPGA

Weinberger Array (NOR Logic)

 


$$F = (A+B+C)D \quad \text{Out} = \overline{A+B+C+D}$$


Gate Matrix

 


Gate Array

 

SOG: Sea-of-Gates

 


Example of SOG Design

 

Physical Layout Skills

1. Widening methods:

 


2. Crossover:




Physical Layout Skills

 3. Dog-bone/Dog-Leg: No need to change layers for crossing




 4. More usage of white space: Rubber forcing




Folding Lines of Diffusion

Example: Full Adder

 


Folding Lines of Diffusion

Example: Full Adder

 


Folding Lines of Diffusion

Example: Sum=A⊕B⊕C

 


Connections of Standard Cells


1. Butting

 


1. Wired

 


3. Feedthrough






 


Transmission Gate Layout Consideration

 

Multiplex

 

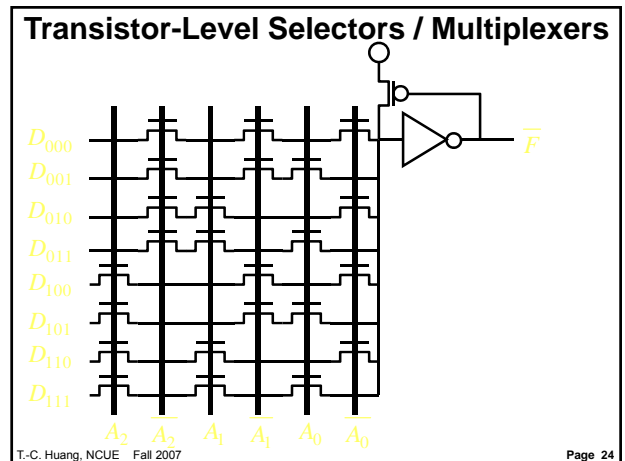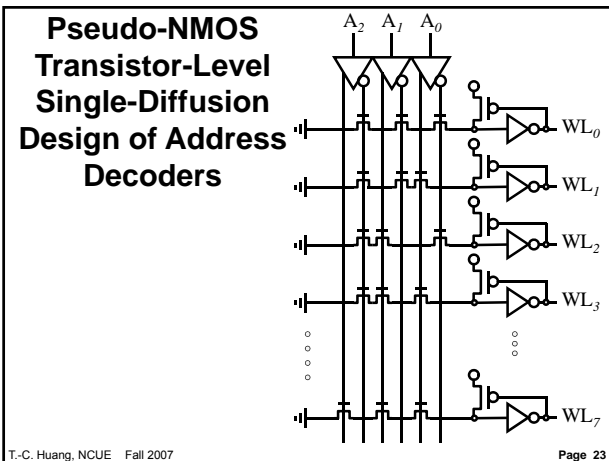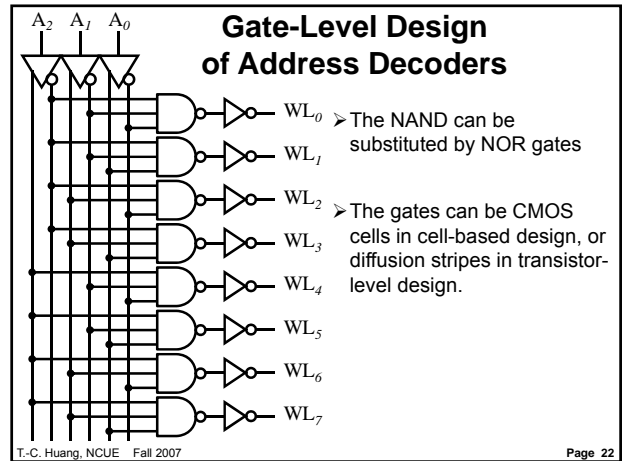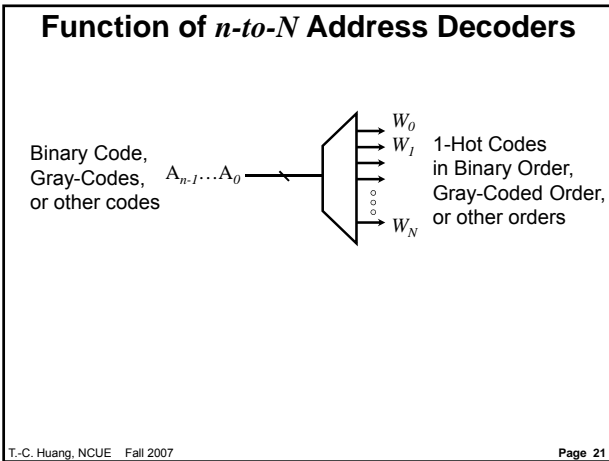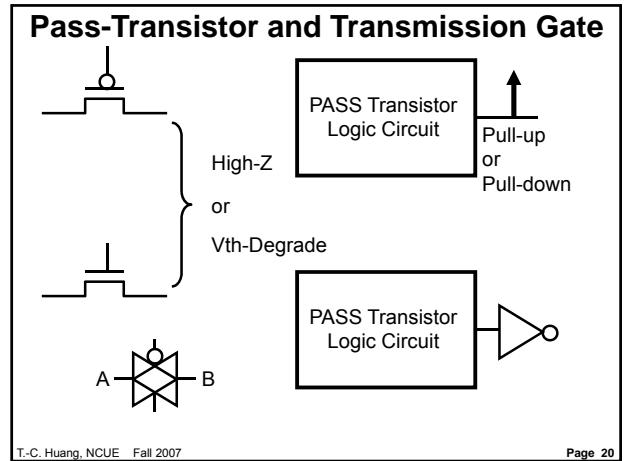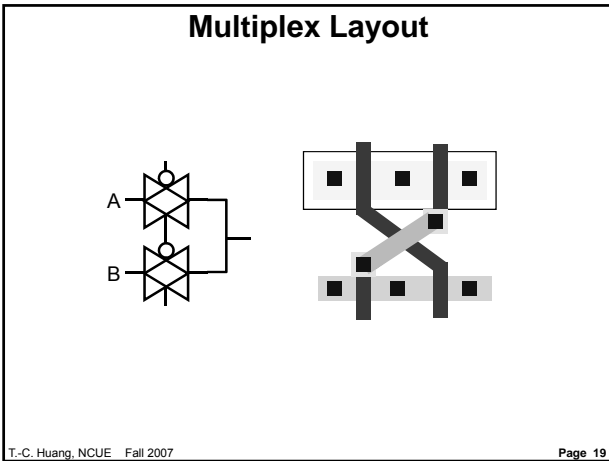

CMOS Logic Structures

1. Conventional Logics
2. RAM/ROM-based Logic (dense, easily configurable)
3. Fully/Partially Complementary Logic (CMOS) (dense, LP)
4. BiCMOS Logic (improving drive, fanout)
5. NMOS-like Logic (high fanin, half transistor count)
6. Source Follower Pull-up Logic (SFPL, '92, improving speed)
7. Pass-Transistor Logic (PTL) ($\rightarrow 1/4$ count, V_t -drop)
8. Transmission-Gate Logic (TGL) (complementary)
9. Clocked CMOS Logic (reducing glitch, speedup)
10. Dynamic CMOS Logic (speedup)
11. Domino Logic ('82)
12. Differential Cascode Voltage Switch Logic (DCVSL, '84, IBM)
13. True Single-Phase Clocked Logic (TSPC, '89)
14. Complementary Pass-Transistor Logic (CPL, '90)
15. Differential Domino CMOS Logic
16. MOS Current-Mode Logic (MCML, '96)

T.-C. Huang, NCUE Fall 2007

Page 25

1. Conventional Logics

Bipolar Junction Transistor (BJT)

- Relay Logic
 - Ladder Diagram, incomplete logic
- Sequentially Accumulated (Computed) Logic
 - Input, calculated, and output in MCU; Very slow applications
- DRL (Diode-Resistor Logic)
 - Pulled by R, almost passive
- TDL (Transistor-Diode Logic)
- TRL (Transistor-Resistor Logic)
- TTL (Transistor-Transistor Logic)
 - Standardized, 0~0.4/2.8~5V
- ECL (Emitter-Coupled Logic)
 - Fast, high power dissipation
- Integrated Injection Logic
 - Basically, a Wired AND logic at the collector; 1972

T.-C. Huang, NCUE Fall 2007

Page 26

2. RAM/ROM-based Logic

A Logic Unit in Some CPLD

ABC	W	X	Y	Z
000	0	0	0	0
001	0	0	1	1
010	1	0	0	1
011	1	0	0	0
100	0	1	0	0
101	1	0	0	0
110	0	0	1	0
111	0	0	0	1


- Universal but exponential size wrt. input count.
- Easily synthesizable
- Flexible and reconfigurable for both RAM and logics.
- Usually utilized in most CPLD.

T.-C. Huang, NCUE Fall 2007

Page 27

3. Standard CMOS Logic Structures

Complementary MOS Logic

 


T.-C. Huang, NCUE Fall 2007

Page 28

 4. BiCMOS Logic Structures

BiCMOS Logic

- Compared with Bipolar Logics:
 - CMOS Logics: Low power ($I_{DDQ} \rightarrow 0$)
 - Poor drive capability
- Basic idea of BiCMOS Inverter:




T.-C. Huang, NCUE Fall 2007

Page 29

4. BiCMOS Logic Structures

A BiCMOS Inverter

 


T.-C. Huang, NCUE Fall 2007


Page 30

5. NMOS Logic Structures

NMOS Inverter

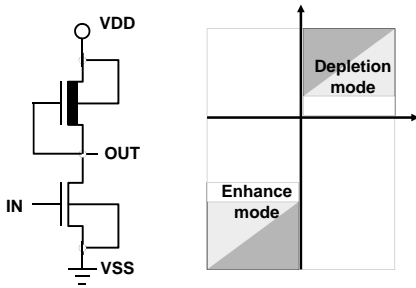


5. Pseudo-nMOS Structures

 

5. NMOS-like Structures


NAND-Type (Pseudo-) NMOS Circuit

 


Body Effect!
Compact, low-power but slower.

5. NMOS-like Logic Structures


NOR-Type (Pseudo-) NMOS Circuit

 

5. Compaction, Leakages & Speed

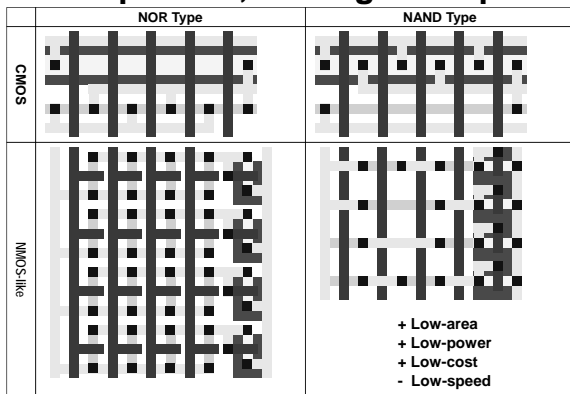

Programmable Logic Array (PLA)

 

7. Pass-Transistor & Transmission Gate

High-Z
or
Vth-Degrade

PASS Transistor Logic Circuit

Pull-up or Pull-down

PASS Transistor Logic Circuit

A B

T.-C. Huang, NCUE Fall 2007 Page 37

Multiplex (review)

A B

C

0 1

A C

C B

Z

A B

T.-C. Huang, NCUE Fall 2007 Page 38

Multiplexer Layout

A B

T.-C. Huang, NCUE Fall 2007 Page 39

Bus Contention

A CA

B CB

Exclusive pulse

More safe!

Ideal multiplexing

Bus Contention!

Another problem in testing: difficult to test the control line stuck-at-1 faults.

T.-C. Huang, NCUE Fall 2007 Page 40

PTL Exclusive OR Gate

Pass-Transistor Logic Synthesis

A B

A B

F

A B

1. Popularly used in modulo-2 logic, such as \oplus in LFSRs
2. Tradeoff btw speed, area and power-dissipation.

T.-C. Huang, NCUE Fall 2007 Page 41

CMOS Logic Structures

Address Decoder using Pass Transistor Logic

D₀₀₀

D₀₀₁

D₀₁₀

D₀₁₁

D₁₀₀

D₁₀₁

D₁₁₀

D₁₁₁

A₂ A₁ A₀

F

T.-C. Huang, NCUE Fall 2007 Page 42

6. SFPL

Source Follower Pull-up Logic

Discharging via Positive-Feedback at Inputs

T.-C. Huang, NCUE Fall 2007 Page 43

CMOS Logic Structures

TTL-Interface Inverter

T.-C. Huang, NCUE Fall 2007 Page 44

CMOS Logic Structures

General Dynamic CMOS Logic

- General Dynamic CMOS Logic:
 - IDD Path is turned off when clock-disabled and/or the output is evaluated when clock-enabled.
- In general:
 - Basic Dynamic CMOS n-Logic.
 - Basic Dynamic CMOS p-Logic.
 - Clocked CMOS Logic.
 - Domino Logic

T.-C. Huang, NCUE Fall 2007 Page 45

CMOS Logic Structures

Basic Dynamic CMOS Logic with n-Logic

T.-C. Huang, NCUE Fall 2007 Page 46

CMOS Logic Structures

Erroneous Evaluation in Cascaded Dynamic n-Logics

- They are evaluated at the same clock edges.
- Even slow evaluation may be impossible if the output has been discharged by pre-charged inputs.

Complementary Clocked, Non-inverting or Zipper

T.-C. Huang, NCUE Fall 2007 Page 47

CMOS Logic Structures

Clocked CMOS Logic (C²MOS)

T.-C. Huang, NCUE Fall 2007 Page 48

CMOS Logic Structures

Tri-State Inverter

A primitive in Verilog: `notif1`

T.-C. Huang, NCUE Fall 2007 Page 49

CMOS Logic Structures

Domino Logic

- The output won't be discharged by pre-charged inputs.
- Evaluation (clock) time should be $> t_r, X \#stages$
- Limitations:
 - Buffer, non-inverting, charge redistribution

T.-C. Huang, NCUE Fall 2007 Page 50

CMOS Logic Structures

Wave Logic

- The timing is much critical.
- Very low immunity.

T.-C. Huang, NCUE Fall 2007 Page 51

CMOS Logic Structures

Domino Logic

- A weak pull-up p-device is used to balance the threshold and to make it static.
- The weak device is fed back -- a latch-version .

T.-C. Huang, NCUE Fall 2007 Page 52

CMOS Logic Structures

NP Domino Logic (Zipper CMOS)

- Dynamic circuit, small area, small parasitic capacitance;
- Glitch-free if designed carefully.

T.-C. Huang, NCUE Fall 2007 Page 53


CMOS Logic Structures

Multi-output Domino Logic (MODL)

T.-C. Huang, NCUE Fall 2007 Page 54


CMOS Logic Structures

Charging Sharing Problem in Domino Logic

 


CMOS Logic Structures

Cascade Voltage Switch Logic (CVSL)

 

- Can be minimized;
- Can be implemented in clocked version, w/ pulled/latched devices.
- Good DC noise immunity => double railed for low voltage.

MOS Current-Mode Logic (CML)

 

- The highest MOS logic recently (1996)
- CVSL and CML provide complement logic outputs.
- Differential pair operates either in the saturation or cut-off regions.
- Current switch occurs at the point of maximum transconductance for both MOSFETs.
- Propagation delay is proportional to the output swing, independent from the supply voltage.
- Constant amount of current is drawn from power supply, independent from the switching activity.
- Much more efforts on dedicate design comparable to the multiple stage OPA design!

MOS Current-Mode Logic (CML)

Example

	B	0	1
A	0	F	F
	1	F	F

